



Activity 6




Label the parts of the electric circuit below.
Drag and drop the words provided.

Power source

Electronic parts

Electrical wires

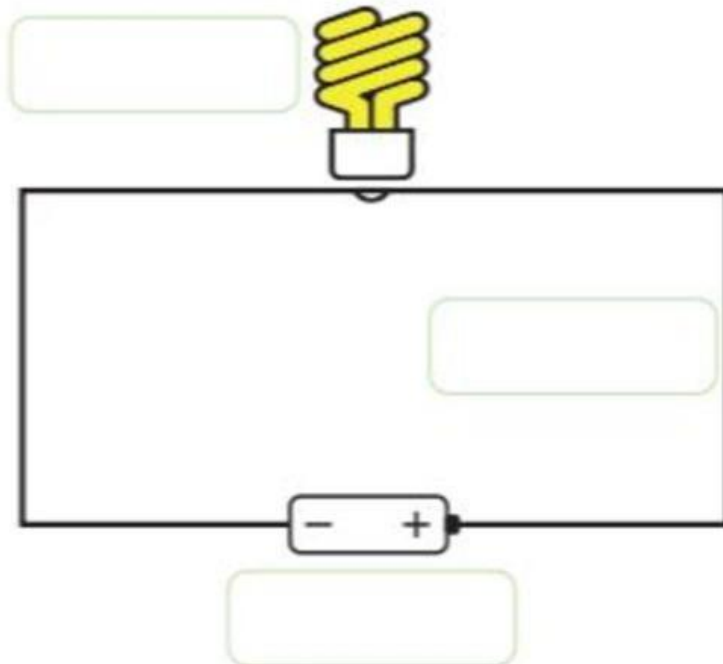

Student Feedback

S
T
R
E
A
M
A

