

ELECTRONIC CIRCUIT

Write the words under the pictures.

switch / battery / wire / bulb



.....



.....




.....



.....

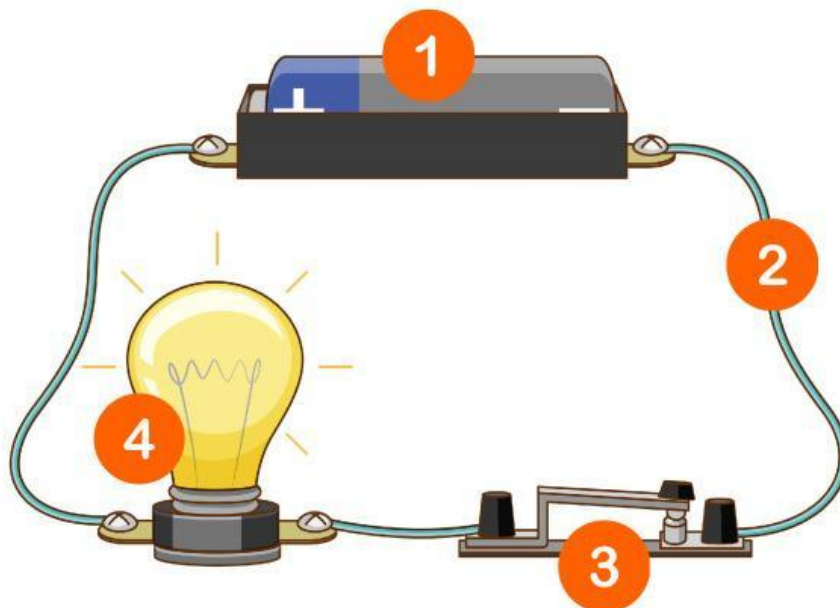Write the components of the electronic circuit below.



1-

2-

3-

4-