

Activity 6




Label the parts of the electric circuit below.
Drag and drop the words provided.

Power source

Electronic parts

Electrical wires

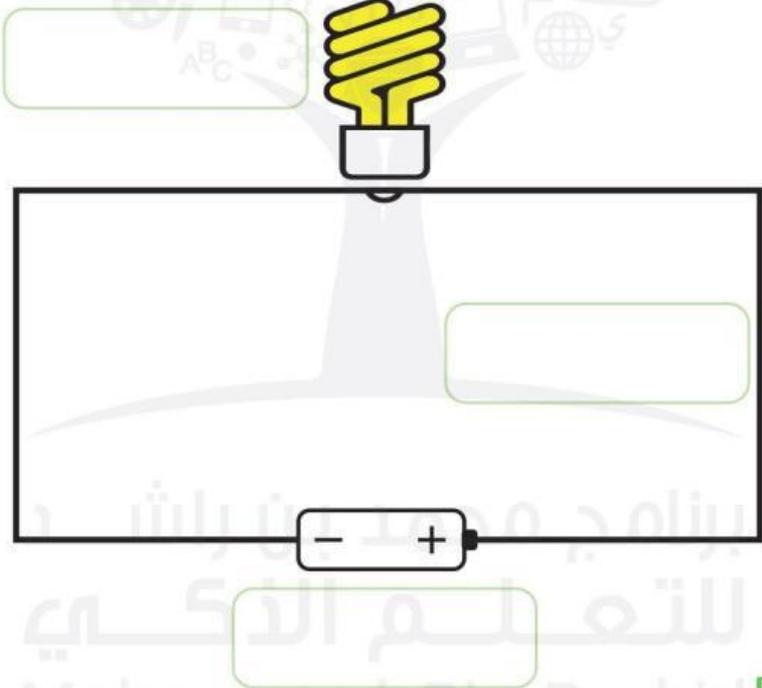

S

T

R

E

A

M

Ai