

Year 4 Science -Term 2 Week 9 Lesson 2

LO: Identify and understand the basic components of an electric circuit.

Fill in the missing words.

loop

complete

energy

path

negative

positive

electricity

1. A circuit is a _ _ _ _ that allows _ _ _ _
to pass through it.

2. Electricity always travels from the _ _
to the _ _ _ _ _ .

3. A circuit will only work if it is _ _ _ _ _

This means it must make a complete _ _ _
otherwise the electrical _ _ _ _ _
cannot flow.