

Year 4 Science -Term 2 Week 9 Lesson 2

LO: Identify and understand the basic components of an electric circuit.

Fill in the missing words.

loop

complete

energy

path

negative

positive

electricity

1. A circuit is a \_\_\_\_\_ that allows \_\_\_\_\_ to pass through it.

2. Electricity always travels from the \_\_\_\_\_ to the \_\_\_\_\_.

3. A circuit will only work if it is \_\_\_\_\_.

This means it must make a complete \_\_\_\_\_ otherwise the electrical \_\_\_\_\_ cannot flow.