



مقرر ماك 805 قسم الكهرباء - دعم فنات الطلاب

Matching –Match the sentences to suit them in the table.

No	Column A	Column B
1-	Formula of power	IN=ZERO Rph1=Rph2=Rph3
2-	Star Connection	$P=V3 \times VL \times IL \times P.F$ $P=V3 \times VPH \times IPH \times P.F$
3-	(AT BALANCE LOAD)	
4-	(AT UNBALANCE LOAD)	to supply and ends connected together.
5-	Delta Connection	
6-	in delta connection Start connect	IN≠ZERO Rph1≠Rph2≠Rph3
7-	in star connection Starts(begins) connect	To the end in delta connection

Teacher: - AHMED SHAHIN

HEAD OF SECTION: -Reda Hadi

HEAD MASTER: SAYED REDA