


Zaporedna vezava porabnikov

1. Rezultate, ki si jih dobil pri merjenju toka z virtualnim laboratorijem, vnesi v tabele.




a) Vezava ene žarnice.

U (V)	I (A)
9 V	

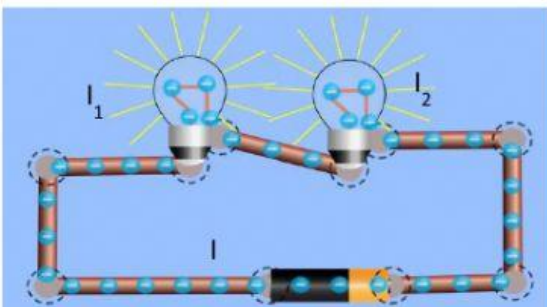

b) Zaporedna vezava dveh žarnic.


U (V)	I (A)	I_1 (A)	I_2 (A)
9 V			

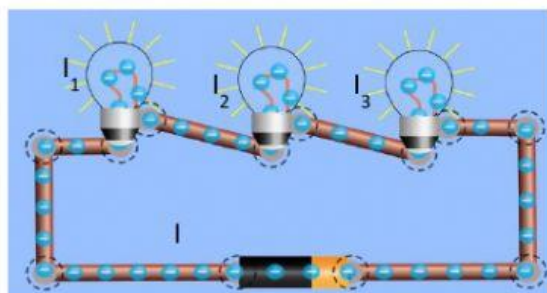

c) Zaporedna vezava treh žarnic.


U (V)	I (A)	I_1 (A)	I_2 (A)	I_3 (A)
9 V				

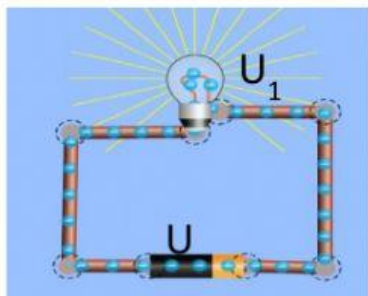2. Rezultate, ki si jih dobil pri merjenju napetosti z virtualnim laboratorijem, vnesi v tabele.




a) Vezava ene žarnice.

U (V)	U_1 (V)

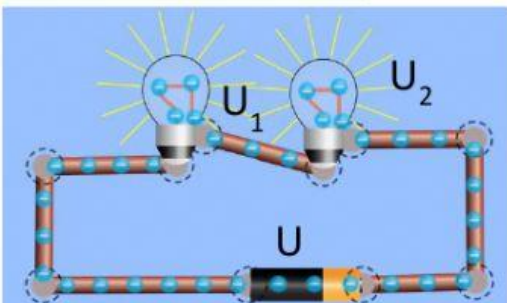

b) Zaporedna vezava dveh žarnic.

U (V)	U_1 (V)	U_2 (V)

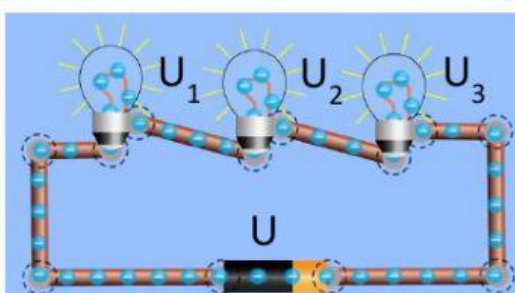

c) Zaporedna vezava treh žarnic.

U (V)	U_1 (V)	U_2 (V)	U_3 (V)