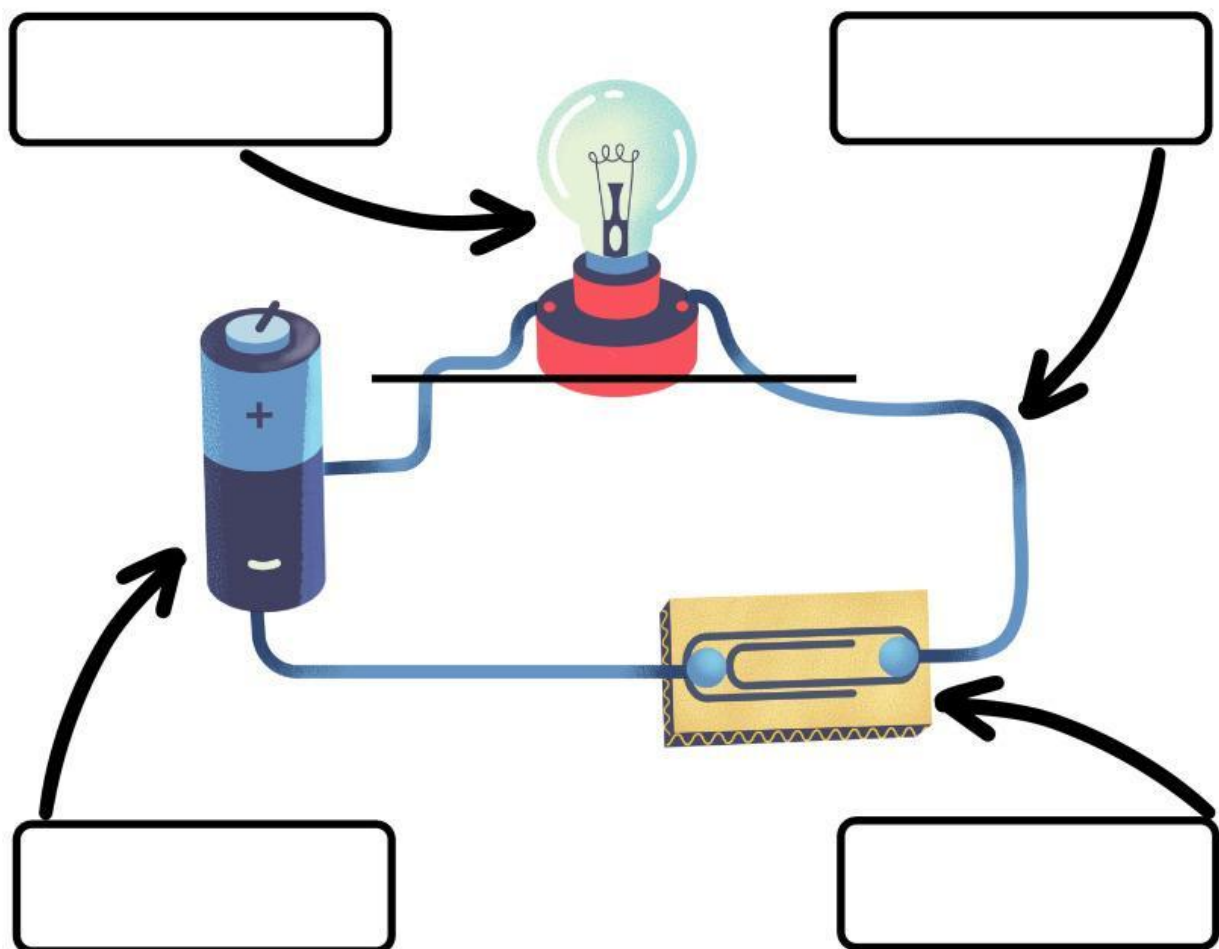


Electrical Circuits

Label the components in the circuit below. Use the words in the word bank to help you.



light bulb
switch

wire
battery