

PARALLEL CIRCUITS. ANSWER SHEET

1.

	R Ω
R1	
R2	
RT	

	V(V)
VR1	
VR2	
VT	

	I(A)
IR1	
IR2	
IT	

2.

	R Ω
R1	
R2	
RT	

	V(V)
VR1	
VR2	
VT	

	I(A)
IR1	
IR2	
IT	

3.

	R Ω
R1	
R2	
R3	
RT	

	V(V)
VR1	
VR2	
VR3	
VT	

	I(A)
IR1	
IR2	
IR3	
IT	

4.

	R Ω
R1	
R2	
R3	
RT	

	V(V)
VR1	
VR2	
VR3	
VT	

	I(A)
IR1	
IR2	
IR3	
IT	

5.

	R Ω
R1	
R2	
R3	
R4	
RT	

	V(V)
VR1	
VR2	
VR3	
VR4	
VT	

	I(A)
IR1	
IR2	
IR3	
IR4	
IT	

6.

	R Ω
R1	
R2	
R3	
R4	
RT	

	V(V)
VR1	
VR2	
VR3	
VR4	
VT	

	I(A)
IR1	
IR2	
IR3	
IR4	
IT	

7.

	R Ω
R1	
R2	
R3	
R4	
RT	

	V(V)
VR1	
VR2	
VR3	
VR4	
VT	

	I(A)
IR1	
IR2	
IR3	
IR4	
IT	

8.

	R Ω
R1	
R2	
R3	
RT	

	V(V)
VR1	
VR2	
VR3	
VT	

	I(A)
IR1	
IR2	
IR3	
IT	

9.

	R Ω
R1	
R2	
R3	
R4	
RT	

	V(V)
VR1	
VR2	
VR3	
VR4	
VT	

	I(A)
IR1	
IR2	
IR3	
IR4	
IT	