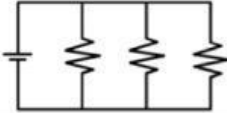
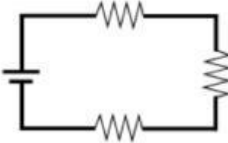


Vocabulary Matching

Name: _____ Date: _____ Grade 4 / _____

Objective: Students will review key energy vocabulary by matching terms with the correct pictures.

Match the correct image to the correct word

Column A	Column B
Resistor	
Wire	
Voltage source	
Switch	
Parallel circuit	
Serious circuit	