



Name: _____


Class: 2A, 2B


Simple Circuit
Science Worksheet#7


---/--/2026


10 Marks

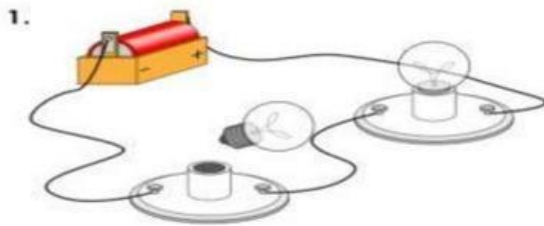
1. Write Will light or Will not light based on the circuit: /10




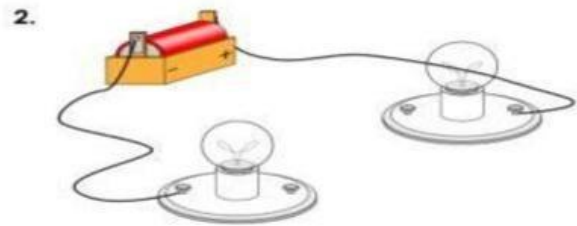

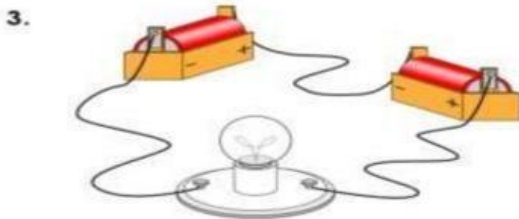

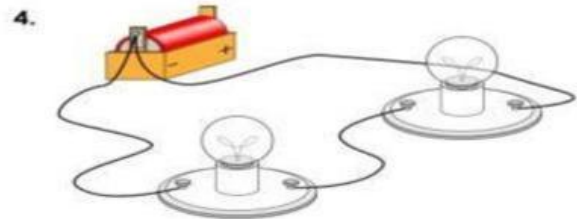

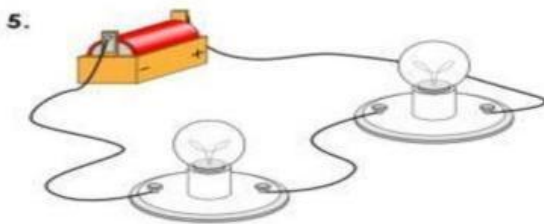

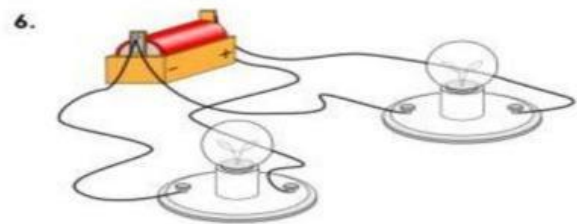



Will light

or

Will not light

