

Frere School –Bethlehem
Science worksheet
1nd grade A , B, C

Challenge Circuits

Determine if the bulb is glowing or not by writing "on" or "off" next to the bulb.

Example:



