
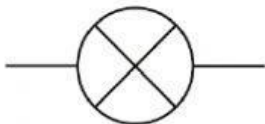

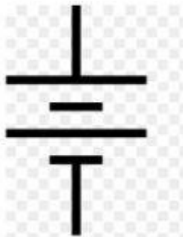






Name: \_\_\_\_\_ Date: \_\_\_\_\_

# SCIENCE WORKSHEETS: PARTS OF AN ELECTRICAL CIRCUIT

## Word Bank

What part?    *Battery,*    *lamp,*    *switch,*    *wire,*

	Symbol!	Which part?
		_____
		_____
		_____
		_____