


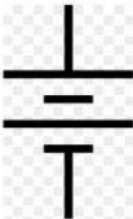






Name: \_\_\_\_\_ Date: \_\_\_\_\_

**SCIENCE WORKSHEETS: PARTS OF AN ELECTRICAL CIRCUIT**

**Word Bank**

**What part?**    *Battery,*        *lamp,*        *switch,*        *wire,*

	Symbol!	Which part?
		_____
		_____
		_____
		_____