

Name: _____

Class: _____

Date: _____

CHECK YOUR PROGRESS

1. These have two names. What are they?




2. What are these called?






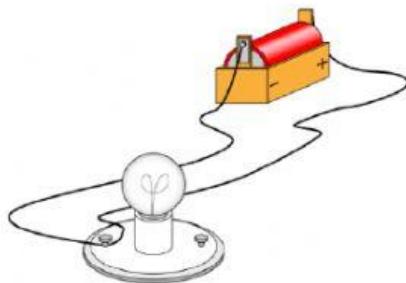3. Will the bulb be **ON** or **OFF** in these circuits?




ON

OFF

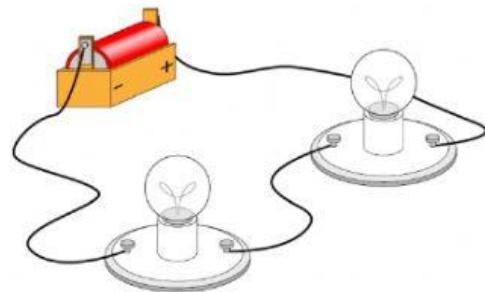


ON

OFF

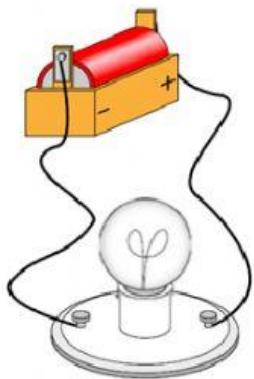

ON


OFF

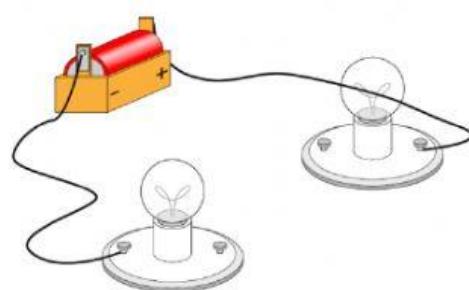

ON


OFF

4. Will these circuits work?

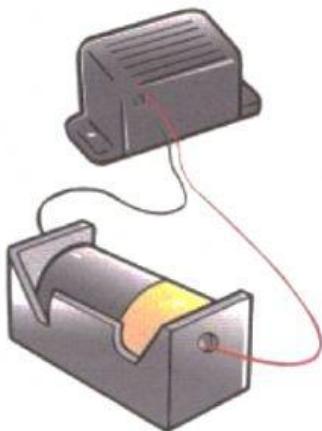


YES

NO

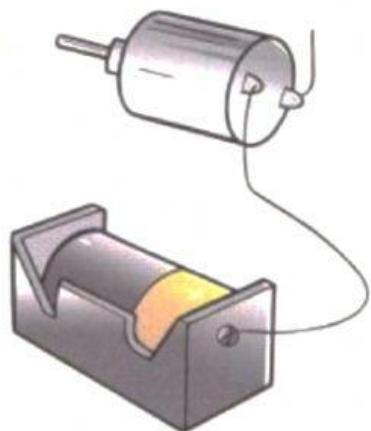

YES

NO

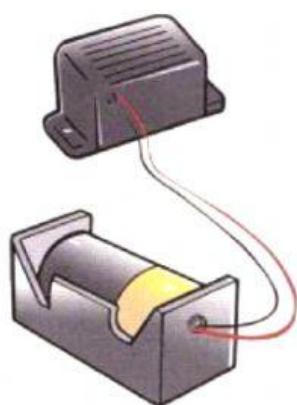

YES

NO