

NAME: _____ GRADE 1- _____ DATE: _____

LO: I can identify the components of a simple circuit.


TASK 1: Complete the statements about the components of simple circuit. Choose your answer from the box.

Conductor	Source	Circuit	Load
-----------	--------	---------	------

1. _____ is a complete path around which electricity can flow.
2. _____ it provides electrical energy or power. Battery is an example of this component.
3. _____ it allows electric current to pass through. Wire is an example of this component.
4. _____ it uses or consumes the power or energy. Bulb is an example of this component.

TASK 2: Label the components of a simple circuit.

- Battery
- Wire
- Bulb

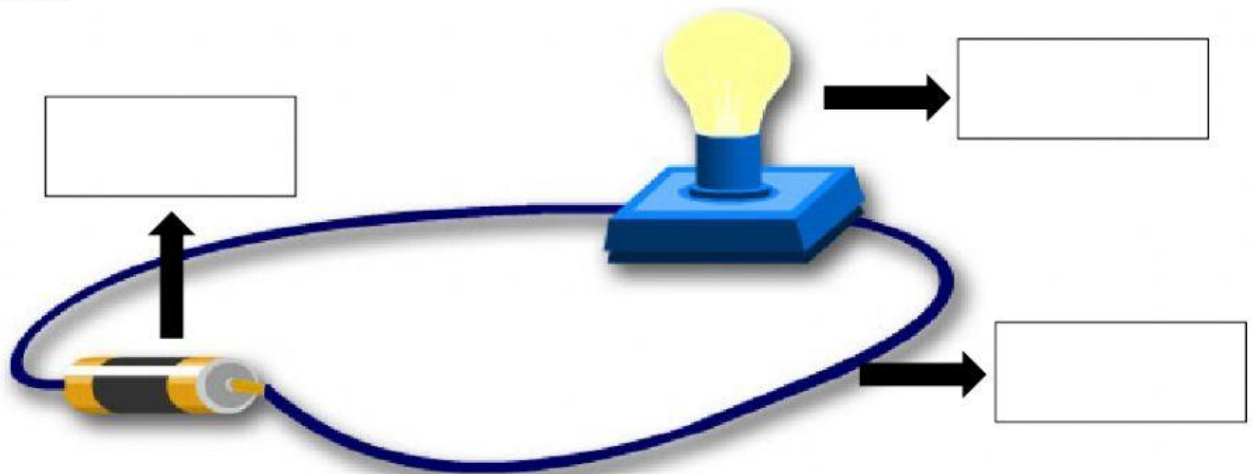

TASK 3: Match the following. Draw a line.

- | | |
|--------------|------------|
| 1. Conductor | a. Bulb |
| 2. Load | b. Battery |
| 3. Source | c. Wire |