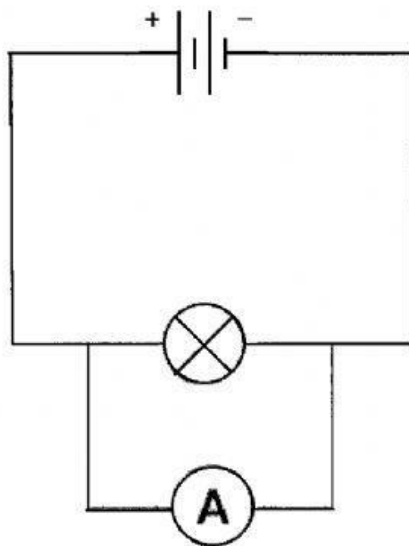


6. Which statement about electric current is correct?

- ☐ it always flows clockwise
- ☐ it gets used up as it goes around the circuit
- ☐ it does not get used up as it goes around the circuit


7. What is wrong with this circuit diagram?



Ammeter - measures Amps

- ☐ there is only one lamp
- ☐ the ammeter should be connected along the series path
- ☐ the ammeter should be connected across the path to make a parallel circuit

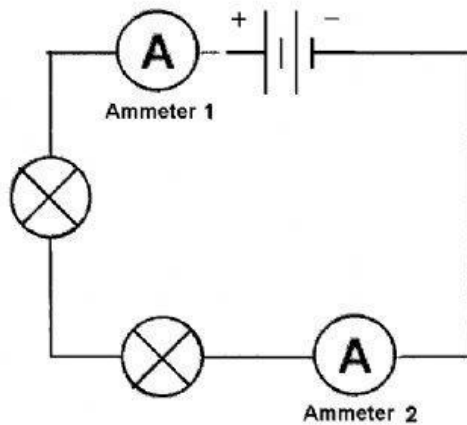8. Which ammeter will have the biggest reading?



- ☐ ammeter 1
- ☐ ammeter 2
- ☐ they will read the same