



A

OR

V



is used to measure current




is connected in parallel



must have high resistance



is connected in series

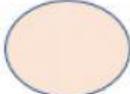

must have low resistance



used to measure the potential difference



LIVEWORKSHEETS