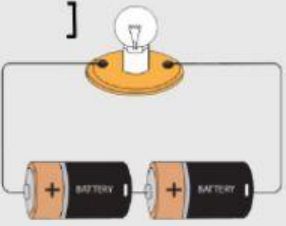
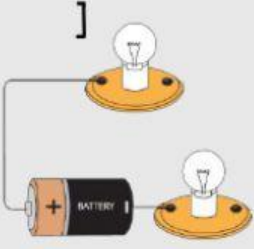
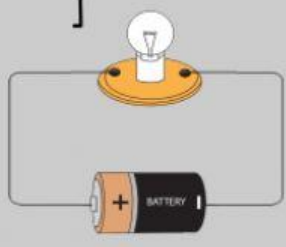
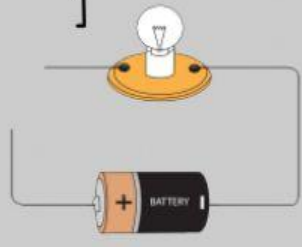
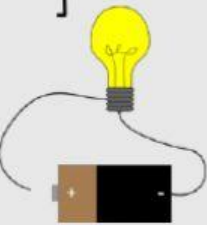
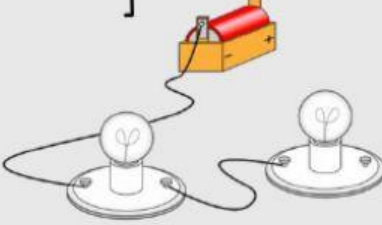
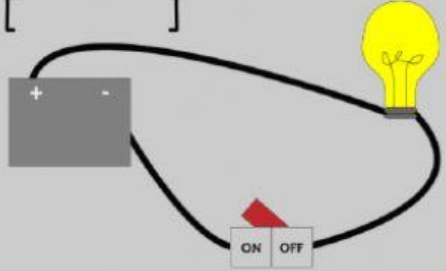
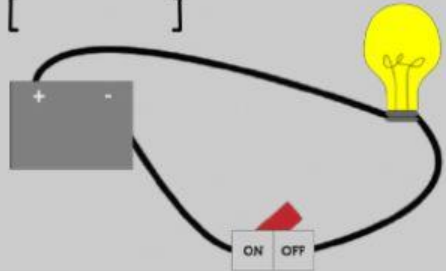
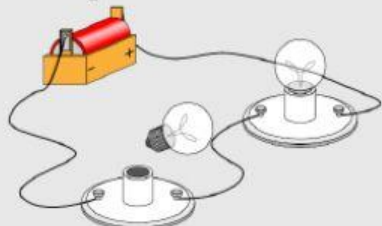
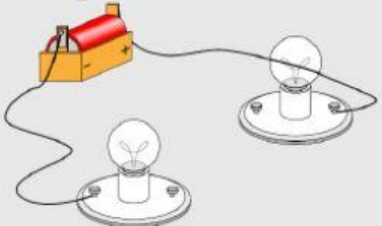


# 2

## SWCS with Micro:bit Lesson 3

**DIRECTION:** Identify whether a circuit will light up or not?

|                                                                                                                    |                                                                                                                      |
|--------------------------------------------------------------------------------------------------------------------|----------------------------------------------------------------------------------------------------------------------|
| 1. [                      ]<br>   | 6. [                      ]<br>    |
| 2. [                      ]<br>  | 7. [                      ]<br>   |
| 3. [                      ]<br> | 8. [                      ]<br>  |
| 4. [                      ]<br> | 9. [                      ]<br>  |
| 5. [                      ]<br> | 10. [                      ]<br> |