Date : .....(Thursday)

Name : ..... Science Year 2 Class : .....

ELECTRICITY : BUILDING AN ELECTRIC CIRCUIT

1. The following is the steps to build an electric circuit. Arrange according to the correct sequence. Label 1,2,3 and 4 in the blanks.

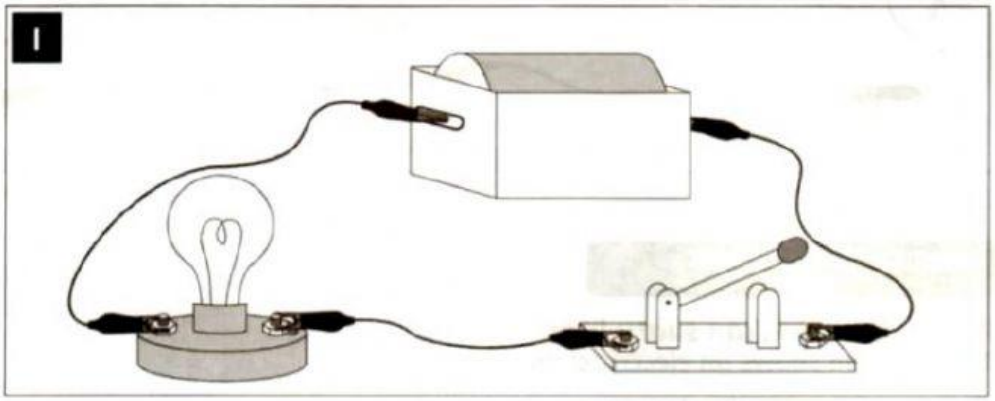

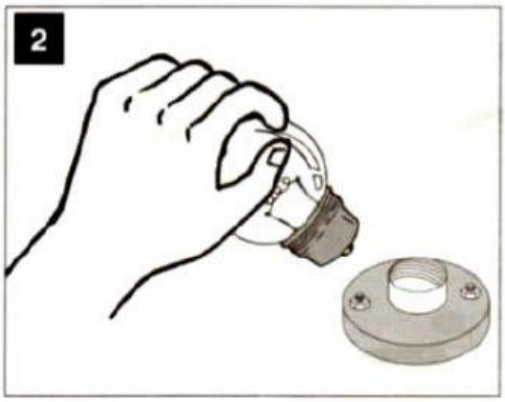

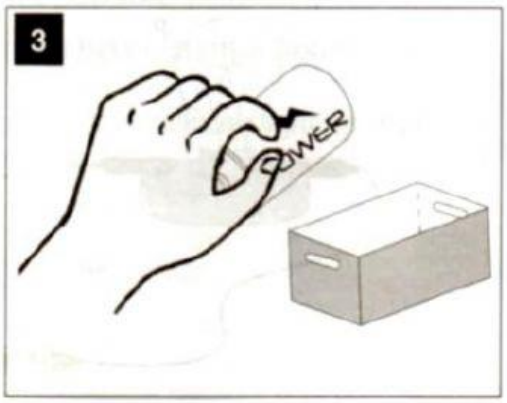

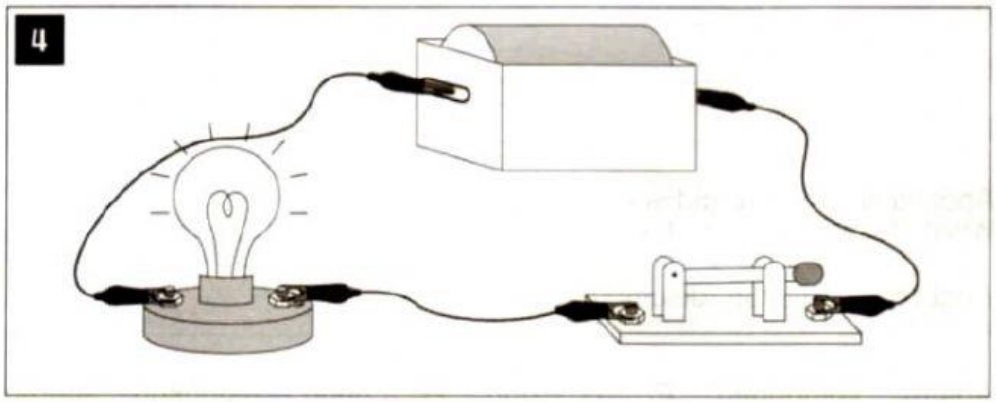

☐ → ☐ → ☐ → ☐

LIVEWORKSHEETS

Date : .....(Thursday)

Name : ..... Science Year 2 Class : .....

2. Observe the circuit. Answer question 2a to 2d is based on the diagram below.

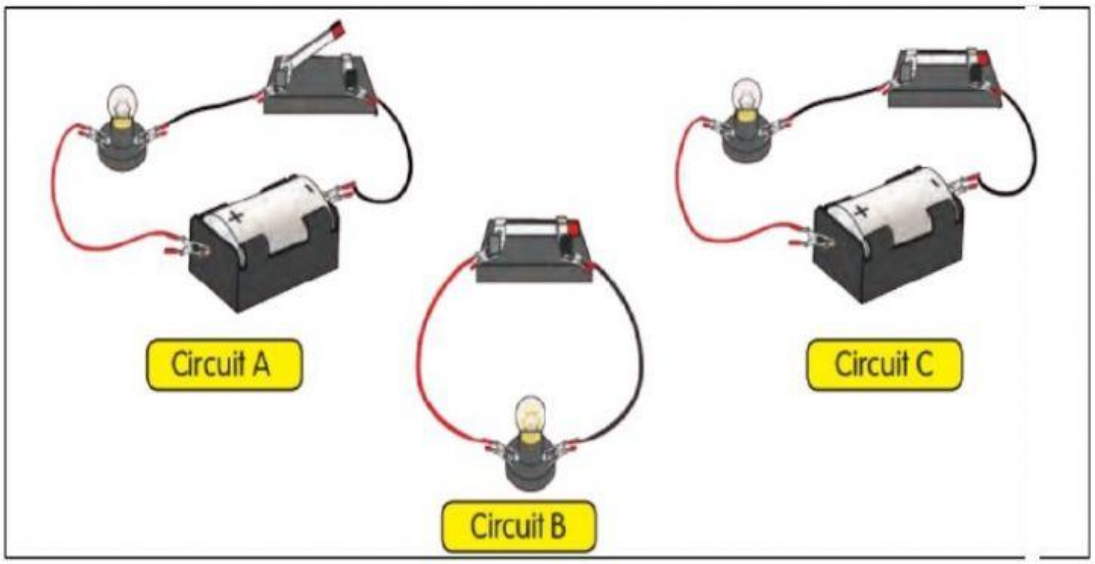

a. Which bulb will light up?

_____

b. Why does the bulb in that circuit light up?

The bulb light up because the circuit is _____.

c. Which bulb will not light up?

_____

d. Why does the bulb in that circuit light up?

The bulb not light up because the circuit is

_____.

LIVEWORKSHEETS