

PLC worksheet 1

Fill in the diagram

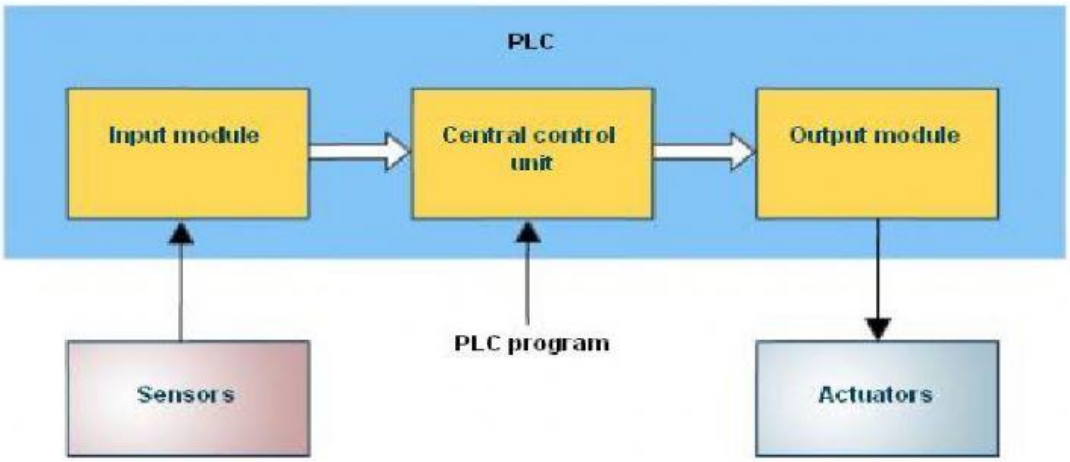


Identify PLC inputs and outputs.

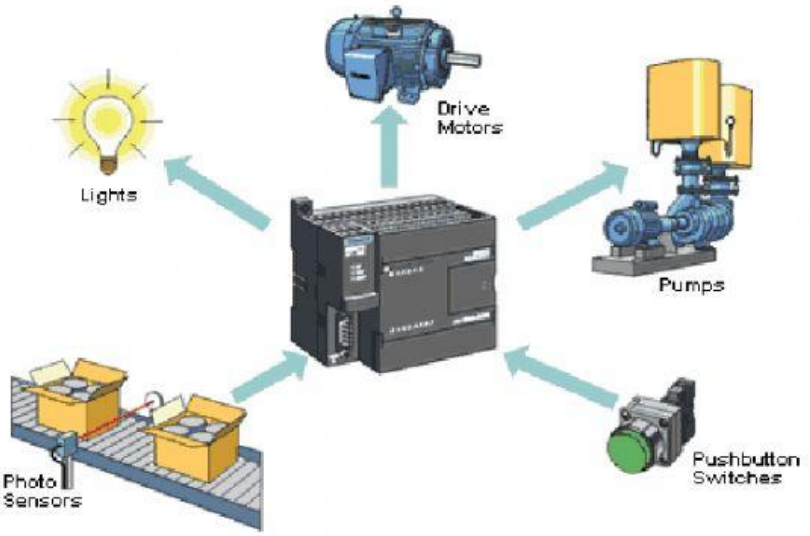


LIVEWORKSHEETS