

WORKSHEETS PART 2



For the Prathomsueksa 6 students of Bangkulad School

Name: _____ **Room:** _____ **Number:** _____

A. Click COMPLETE if the sentence is about a complete circuit and INCOMPLETE if the sentence is about an incomplete circuit.

1. The switch is turned on. **COMPLETE** **INCOMPLETE**
2. Electricity can not flow. **COMPLETE** **INCOMPLETE**
3. It is also called an open circuit. **COMPLETE** **INCOMPLETE**
4. The bulb lights up. **COMPLETE** **INCOMPLETE**

B. Match the words in column A to the symbols in Column B. Connect them by drawing lines.

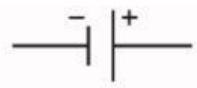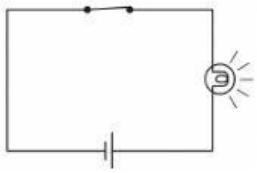COLUMN A	COLUMN B
5. on switch	A. 
6. connecting wire	B. 
7. battery	C. 
8. off switch	D. 
9. bulb	E.
10. simple electric circuit	F. 

LIVEWORKSHEETS