
Match each word to the circuit.

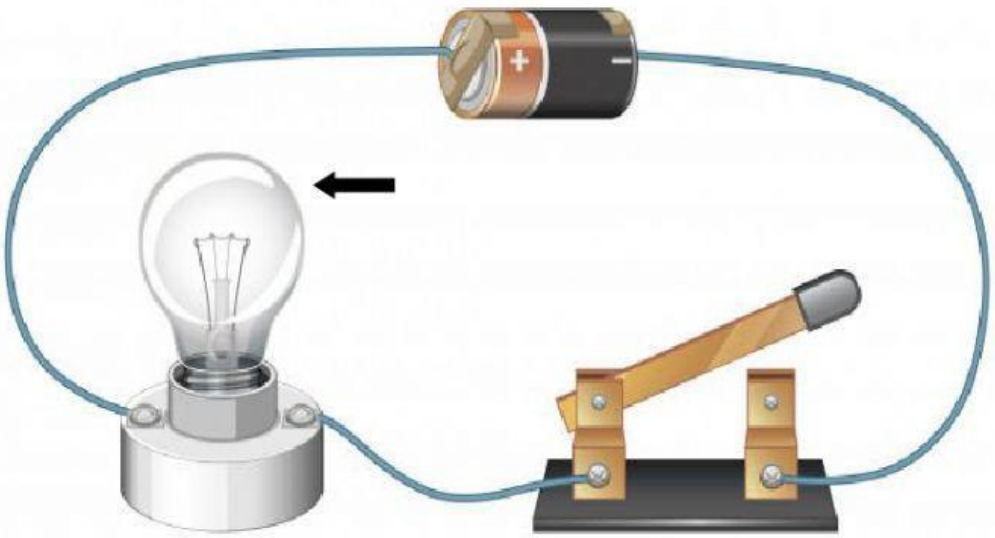

bulb
switch
wire
cell
bulb holder

Match the name to the picture and the function.

wire		**Turns the circuit on or off**
buzzer		**Moves something move**
bulb		**Stores the electricity**
motor		**Connects the parts of a circuit**
cell		**Lights up**
switch		**Makes a sound**

LIVEWORKSHEETS