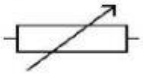
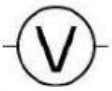
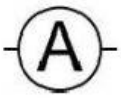
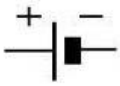
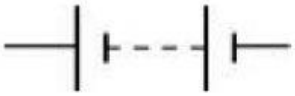
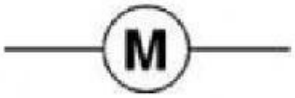
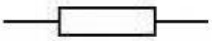
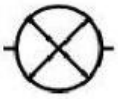
Name: Date:

Grade 8 Circuit symbols Lesson check

Match the symbol to the electrical component it represents.

Symbol	Component
	ammeter
	cell
	battery
	voltmeter
	variable resistor
	motor
	bulb
	switch
	resistor

LIVEWORKSHEETS