Applied English

Unit 4 – Cause and Effect

Review of Week 2 Term 2

Switches and Relays

1. Drag and drop the electronic symbol words under the correct images below.

conductor	lamp	buzzer
bell	battery	terminal
earth	switch	fuse

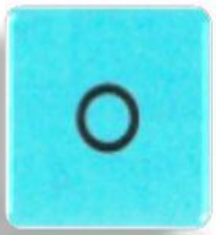

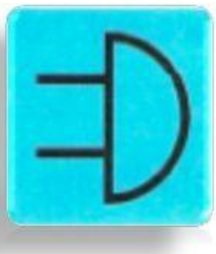

LIVEWORKSHEETS

2. Label the two diagrams below with the correct words from the box.

battery	buzzer	spring
switch	terminal	wire

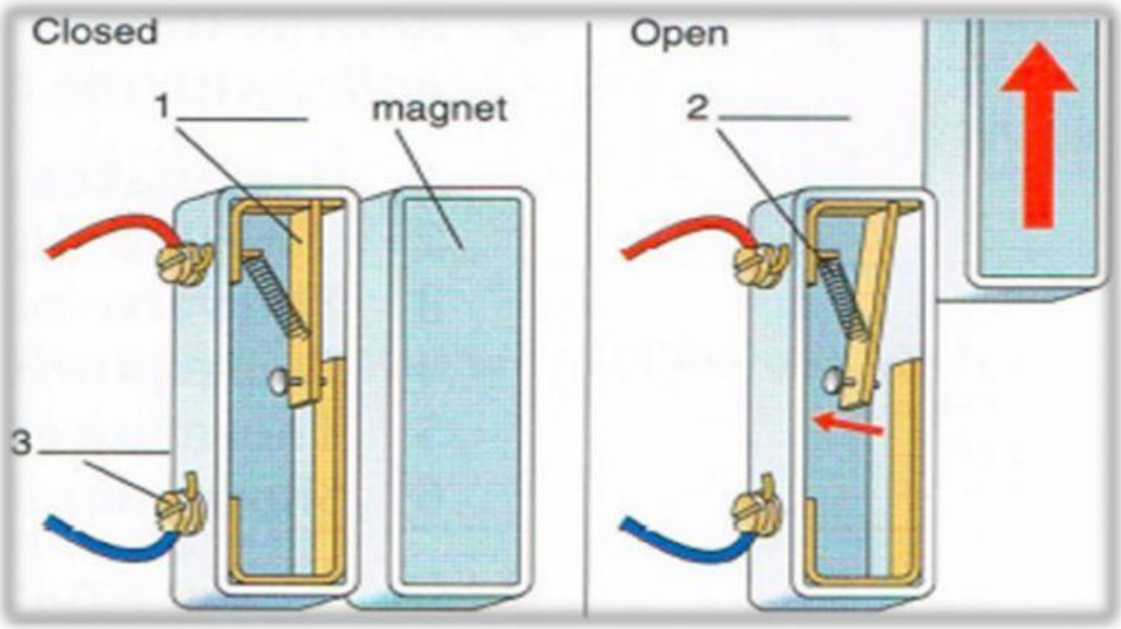

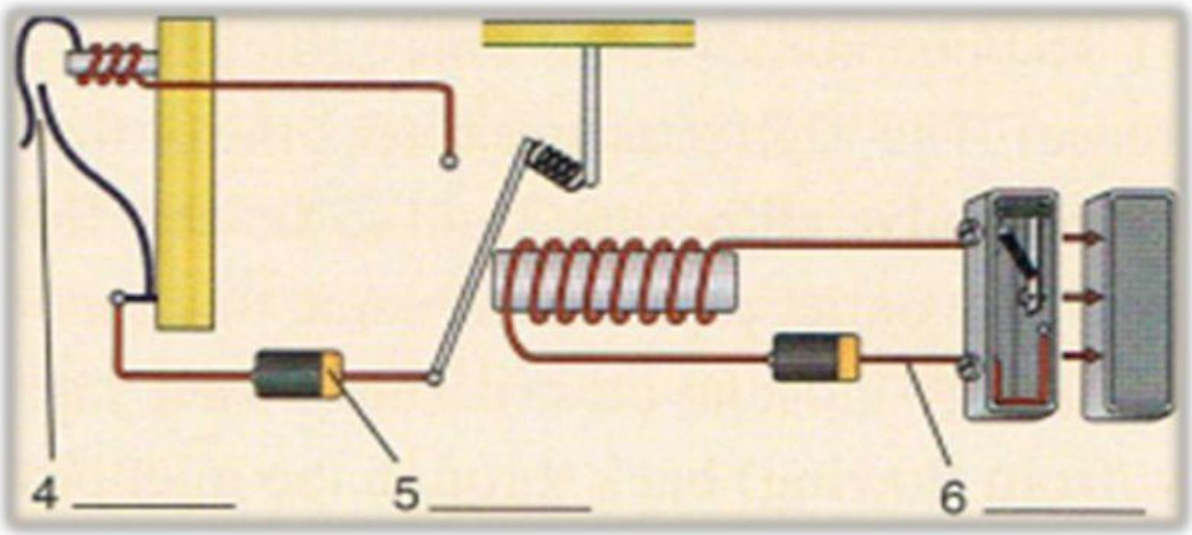

LIVEWORKSHEETS

3. Label the parts of a circuit breaker with the correct words from the box.

terminal	fixed contact	switch	moving contact	electro-magnet	terminal	catch

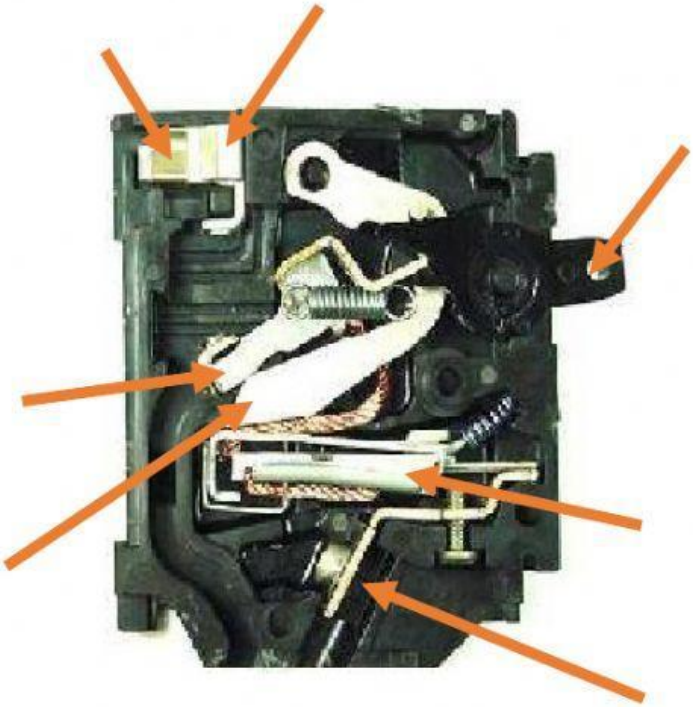

LIVEWORKSHEETS