Parts of a circuit

Choose the name of the following images:

1. _

2. _

3. _

4. _

LIVEWORKSHEETS

5. _

6. _

7. _

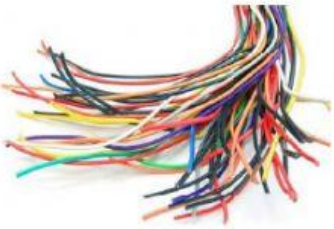

LIVEWORKSHEETS