Verifying Ohm's law in series and parallel circuits

Activity 8

Theory

Look at the picture below. Which LED is connected correctly? The red LED or the blue LED? Explain.

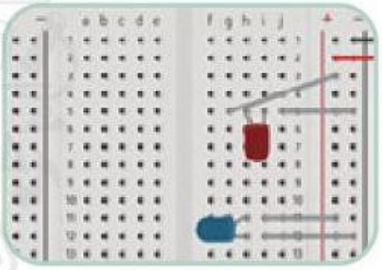

LIVEWORKSHEETS