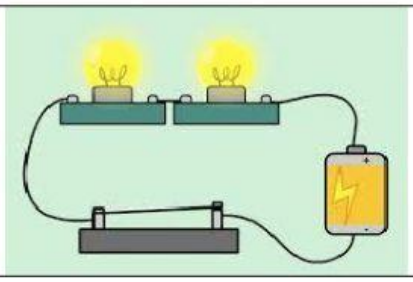
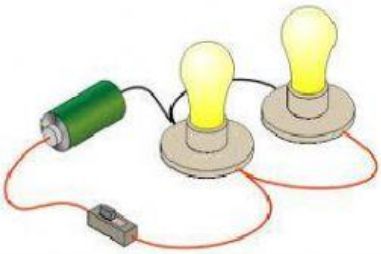
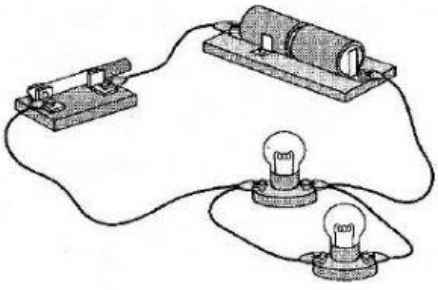
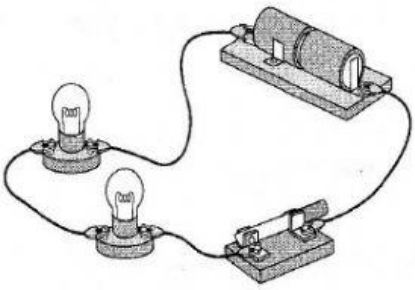
Name :

Class :

Name the circuit below correctly, 1 series circuit or 2 parallel circuit.

1.		2.	
3.		4.	
5.		6.	
7.		8.	

LIVEWORKSHEETS

LIVEWORKSHEETS