ADUVIE INTERNATIONAL SCHOOL, 08089394474

WORKSHEET ON ELECTRICITY (Circuit and Mains Electricity)

NAME _____ **DATE** _____

SUBJECT: SCIENCE **CLASS**: YEAR 3 EMERALD_____

INSTRUCTION: Fill in the blanks by using the helping words

watches	bulbs	mains	switches	kettles
wires	electricity	fires	buzzers	burns
toasters	batteries	care	shocks	circuit

1. Electricity must be used with _____ as it can cause:
   - Electric _____
   - _____
   - _____
   -
2. Electricity comes from the _____ and _____ or cells.
3. Electricity from battery is used by things such as:
   - Toy cars
   - _____
4. Electricity from the man is used by things such as:
   - Electric _____
   - Electric _____
5. Electricity flows through a path called a _____, which may be made up of:
   - Cells or batteries that push _____around the circuit.
   - _____ that close or open the circuit.
   - _____ that connect parts of the circuit.
   - _____ that use electricity to give off light.
   - _____ that use electricity to make sounds.