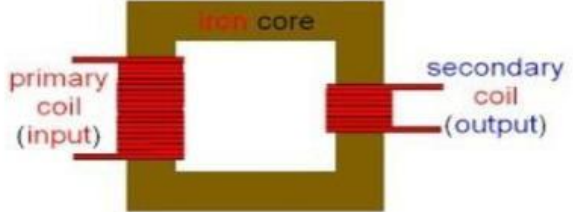
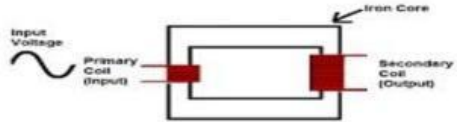
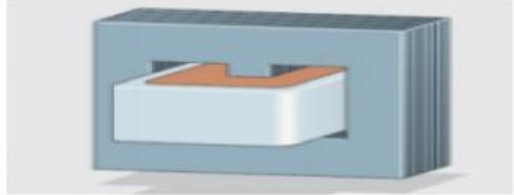
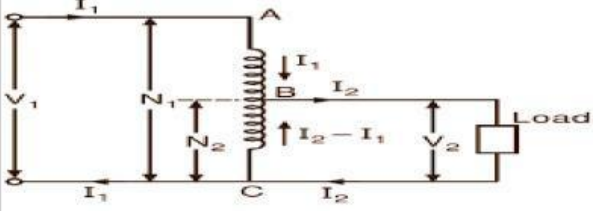


اسم الطالب:-

الرقم الاكاديمي:-

شعبة: 4كهر3

In the table shown, match the picture with the appropriate words shown?

No	Words	Picture
1-	Step-up Transformer	
2-	Step-down Transformer	
3-	Autotransformer	
4-	Core type Transformer	
5-	Shell type Transformer	

Teacher: AHMED SHAHIN

HEAD OF SECTION: REDHA HADI

HEAD MASTER: SAYED REDA