EQUIVALENT RESISTANCE

Identify if resistors are located in series, parallel o it is a mixed arrangement (series and parallel together) and calculate the equivalent resistance (REq) of the following circuits.

Ex.16

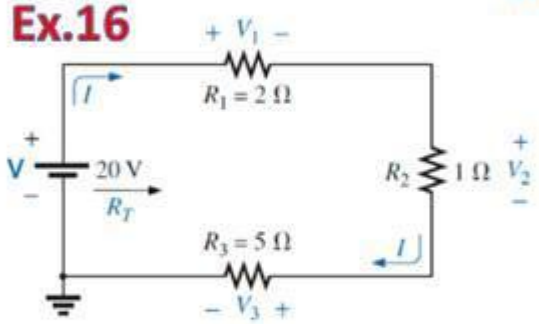

Series

Parallel

Mixed

R_{Eq} = Ω

Ex.17

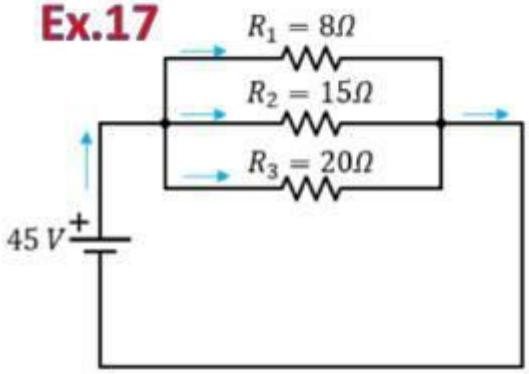

Series

Parallel

Mixed

R_{Eq} = Ω

Ex.18

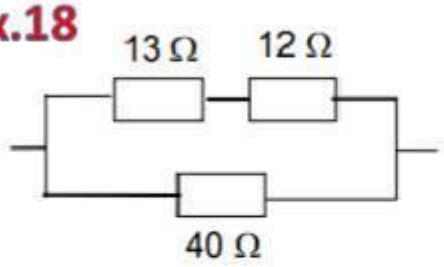

Series

Parallel

Mixed

R_{Eq} = Ω

Ex.19

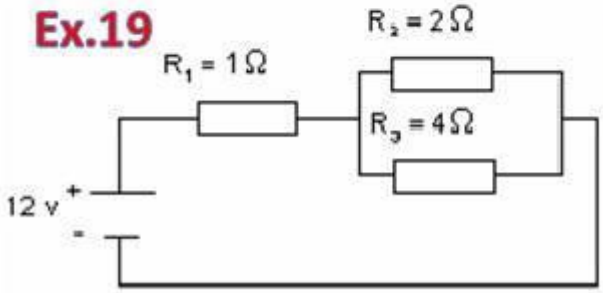

Series

Parallel

Mixed

R_{Eq} = Ω

LIVEWORKSHEETS