
Name: .....

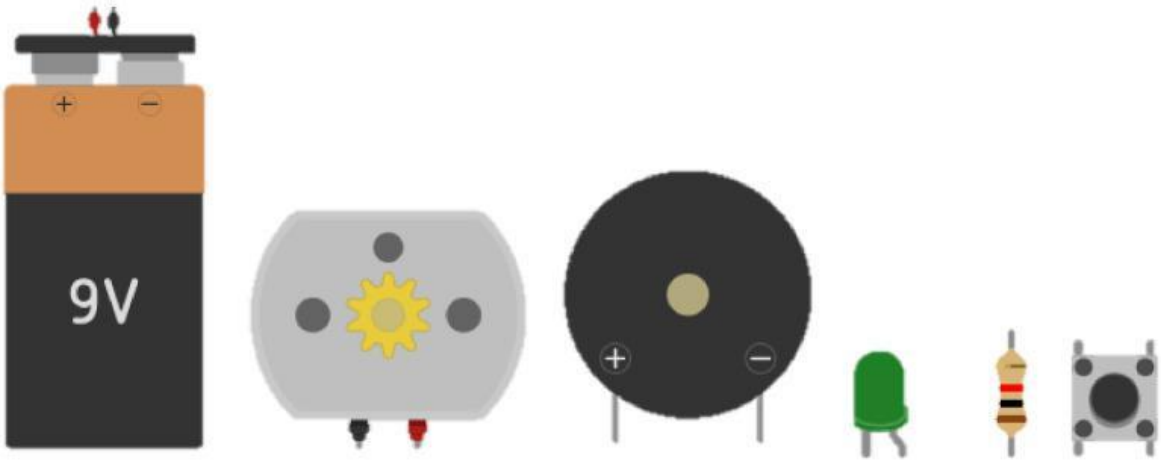1- Connect every electrical component with its name:



LED	**Buzzer**	**Resistor**	**Voltage Source**	**Push button**	**Motor**


LIVEWORKSHEETS


2- Connect every electrical concept with its meaning:


Voltage	**The flow of electricity through an electrical conductor**
Electric Current	**A measure of the opposition to the flow of current in an electrical circuit.**
Resistance	**The "pressure" that pushes electricity through a conducting loop**


LIVEWORKSHEETS

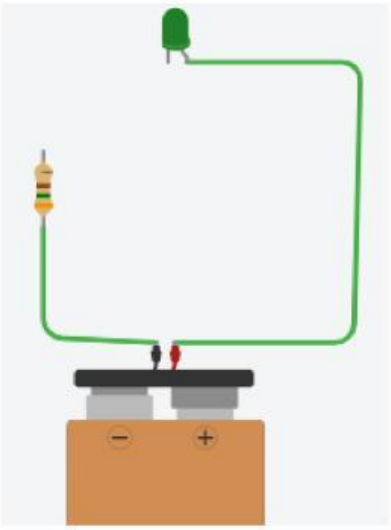3- Determine which circuit will produce light by the LED:



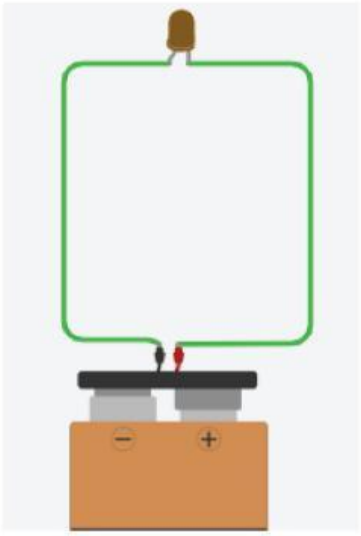

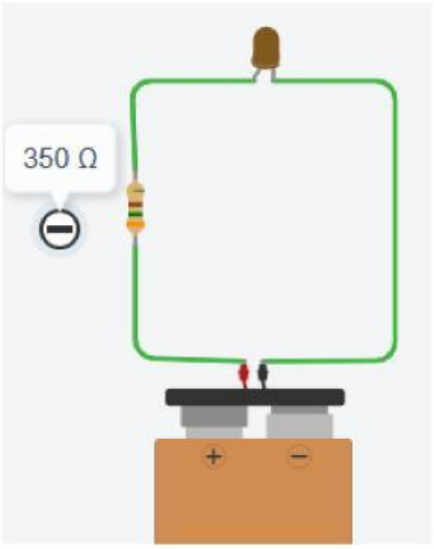

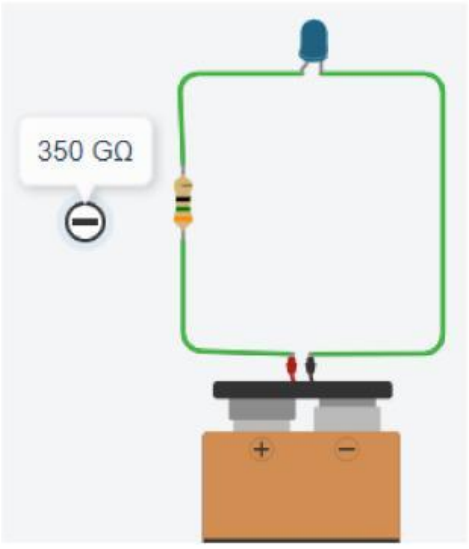

LIVEWORKSHEETS