
Electrical Circuits

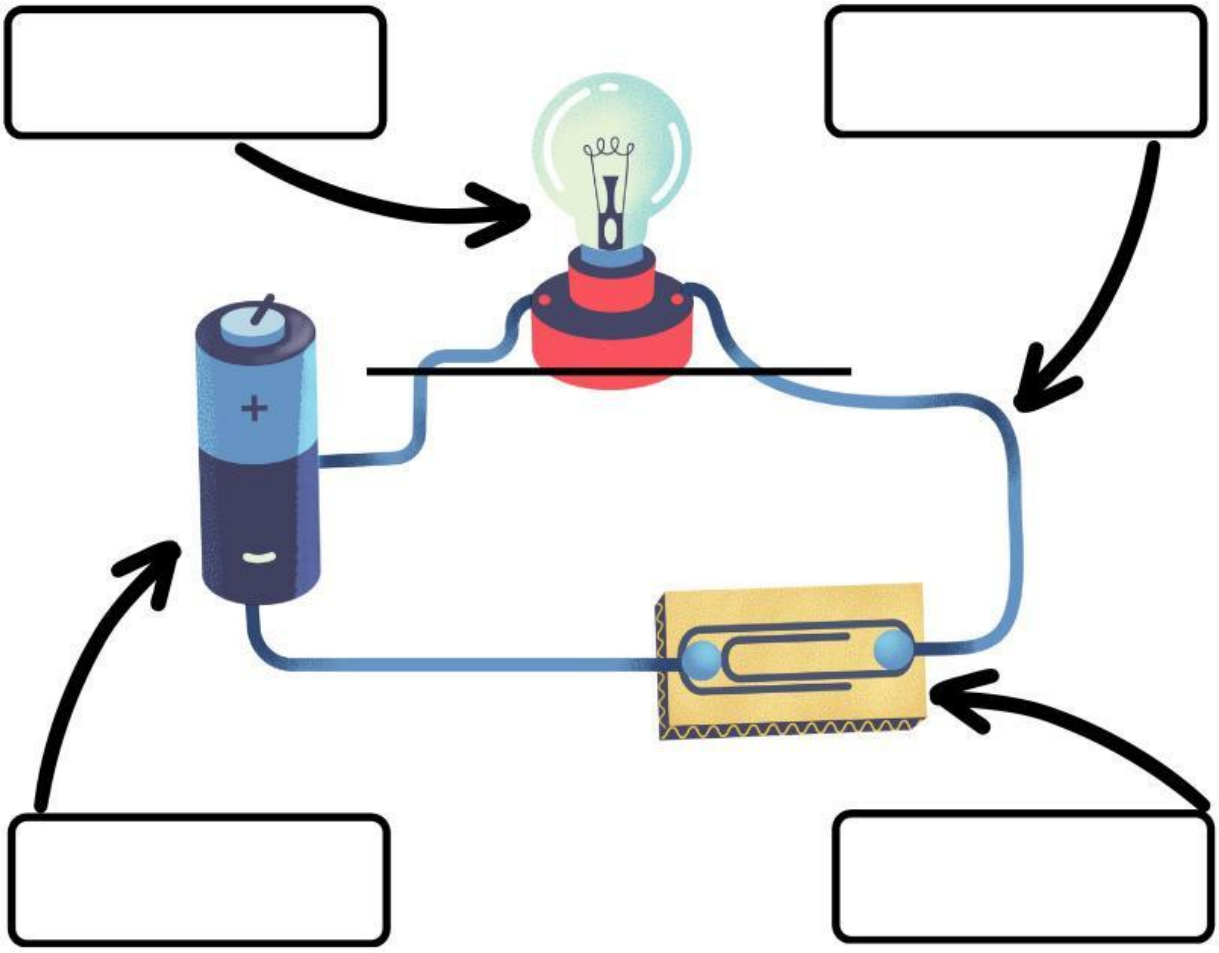Label the components in the circuit below. Use the words in the word bank to help you.



light bulb	wire
switch	battery

LIVEWORKSHEETS