Name: _____

Drag the correct symbol/ picture.

COMPONENT	SYMBOL
1 dry cell	
2 dry cells	
3 dry cells	
Open switch	
Close switch	
1 bulb	
2 bulb	
Series circuit	
Parallel circuit	

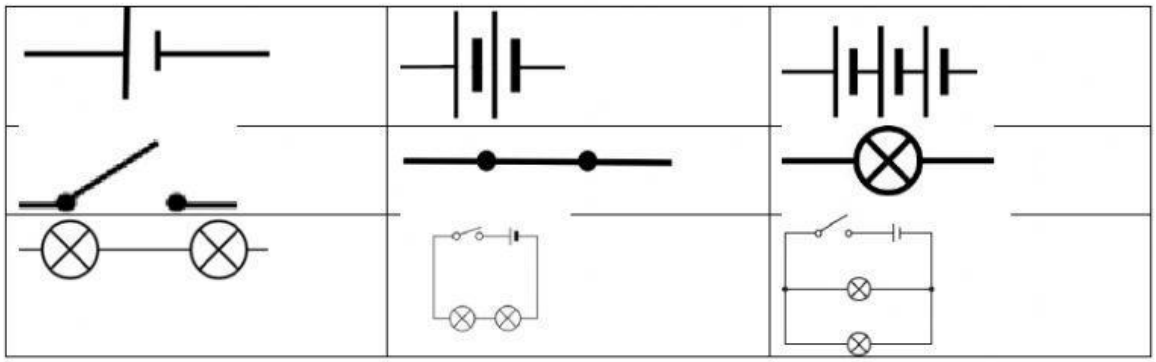

LIVEWORKSHEETS

LIVEWORKSHEETS