EFFECTS OF ELECTRIC CURRENT

Choose the correct answer from the drop down menu

A	B
Heating coil	
Fuse wire	
When resistors are connected in parallel, each resistor will get.....	
W=.....x.....	
In incandescent lamp, the bulb is evacuated in order to.....	
High energy efficient lamp	
When 10 resistors of 2Ω each are connected in parallel,effective resistance R=.....	
Choose the wrong one related to Power	

LIVEWORKSHEETS