What converts a DC signal into and AC signal at a predetermined frequency?

1. Transistor
2. Zener Diode
3. Oscillator
4. Thyristor

LIVEWORKSHEETS

Multivibrator


phase-shifted oscillator


Wien-brigde oscillator


Hartley oscillator


Colpitts oscillator


Pierce oscillator

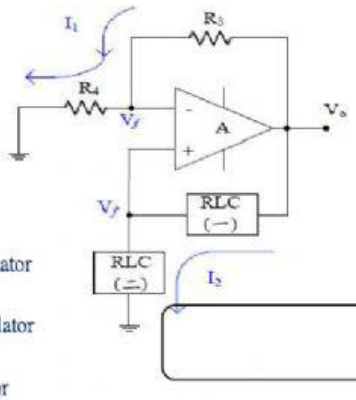


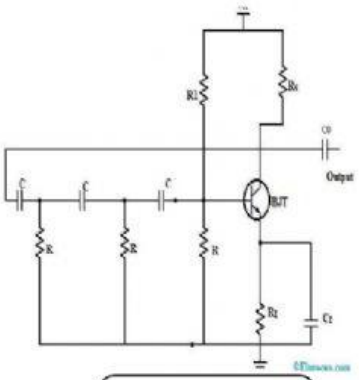

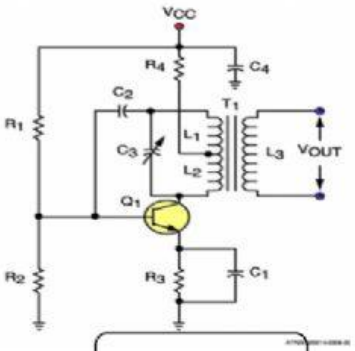

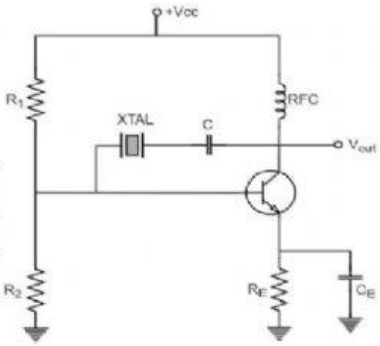

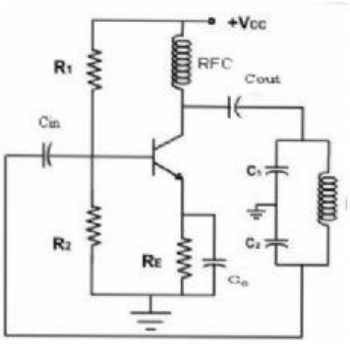

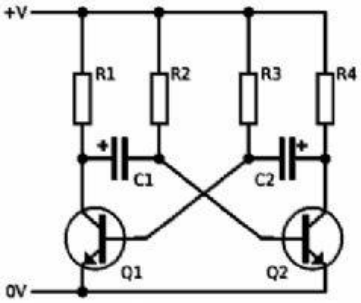

Name

No.

LIVEWORKSHEETS