


School name.....

Student Name.....Student No.....Class

REF03004

Connect single phase fixed wired equipment in refrigeration

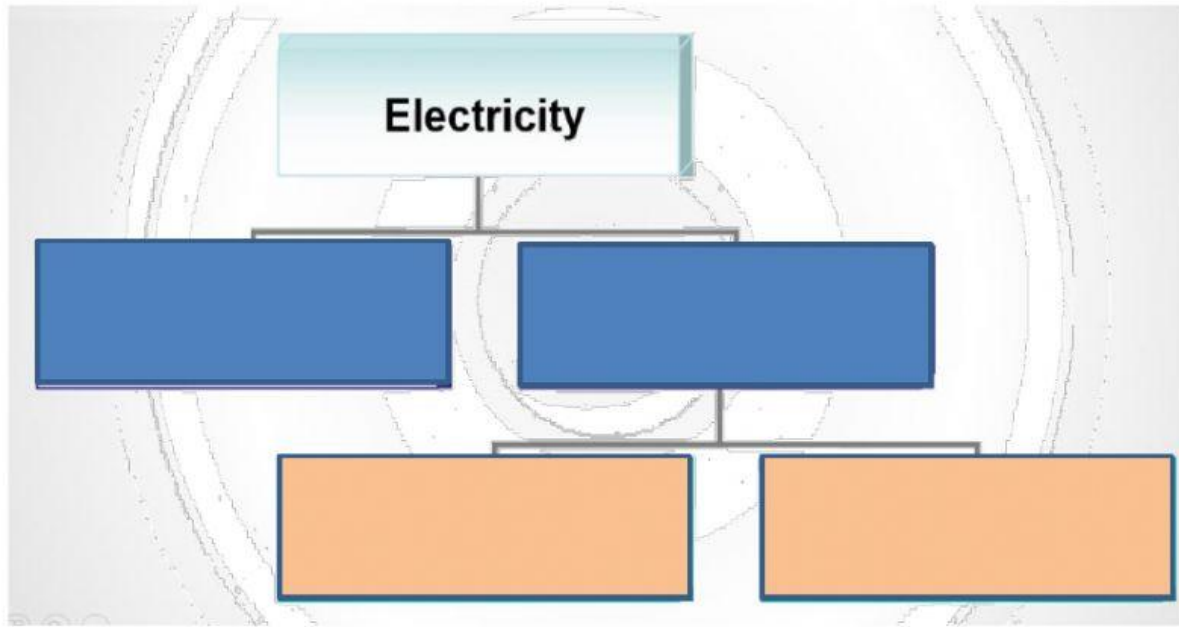Complete the figure shown by the words below



Static Electricity

Current electricity

Direct current

Alternating current