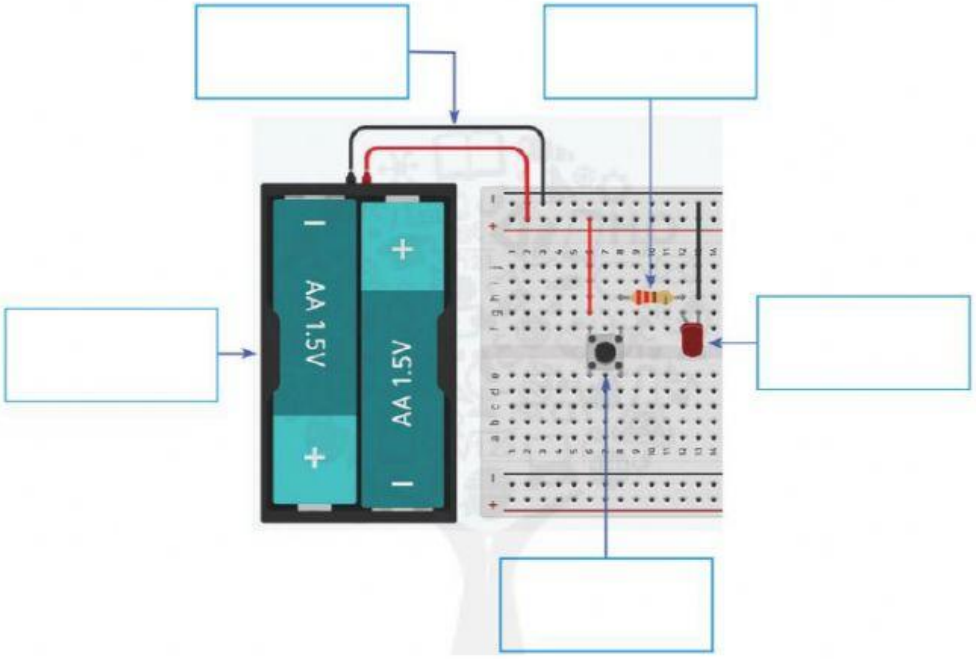


Chapter1: Circuit construction

Label the figure below using the words below:

Name:

push button	load	voltage source	wires



LIVEWORKSHEETS