Activity 7

Look at the two circuits below. Which one is series, and which one is parallel?

Circuit 1

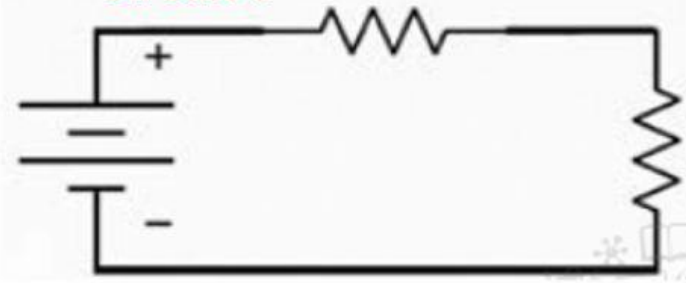

Circuit 2

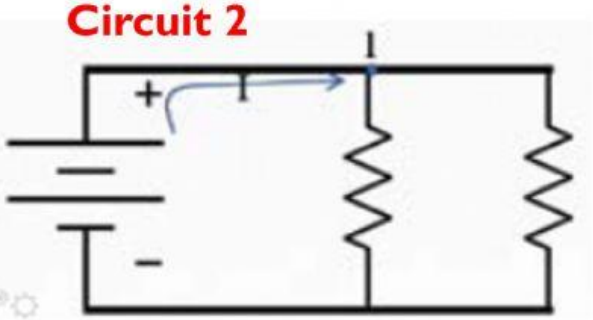

- ❑ Series Circuit
- ❑ Parallel Circuit

- ❑ Series Circuit
- ❑ Parallel Circuit

Smart Learning Program

What will happen to the current when it reaches point (1) in Circuit 2?

- ❑ the current will be distributed over the paths. It will have two ways to flow
- ❑ the current will be in one path. It will have one way to flow
- ❑ Nothings will happen .

LIVEWORKSHEETS