Current Voltage series

In a series circuit which of the following is the same throughout the circuit

In a series circuit which of the following will vary based on the resistor

This type of circuit only has one path for current to flow.

LIVEWORKSHEETS