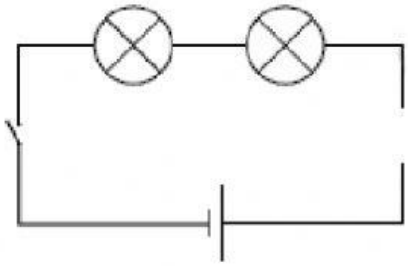
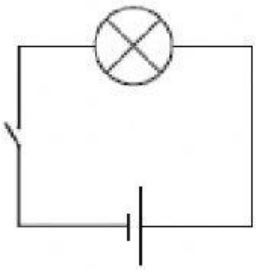
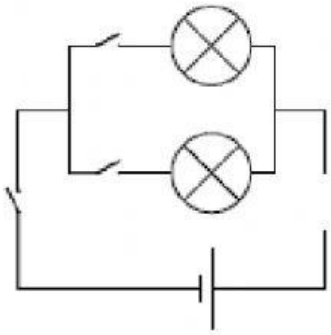
Activity 14

Ahmed and Mariam are learning about **open** and **short circuits**.

Help them to choose which circuits will work and which will not.

Circuit Image	Will the circuit work?	
	Yes	No
		
		
		

LIVEWORKSHEETS