
Name:_____ Date:_____

Electric circuit

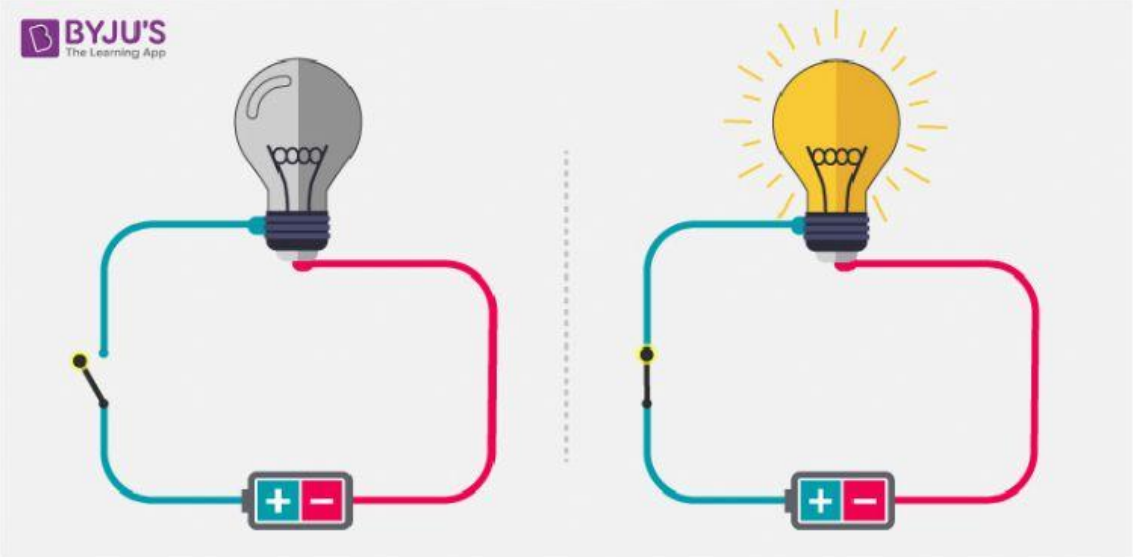

Circuit A Circuit B

1. Which of the circuit above is a complete circuit?

2. What do you think will happen if the circuit is complete? Give reason.

LIVEWORKSHEETS