
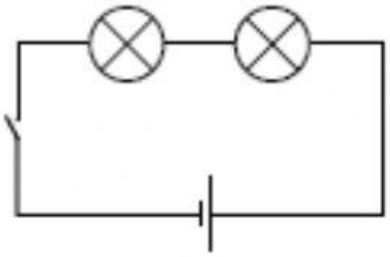
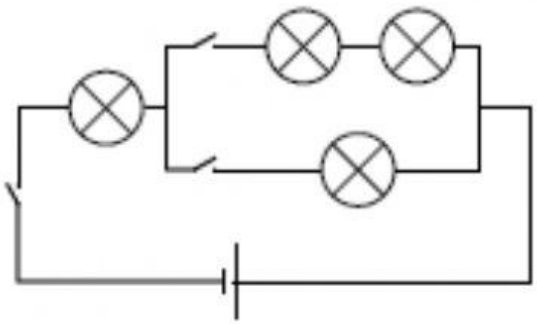
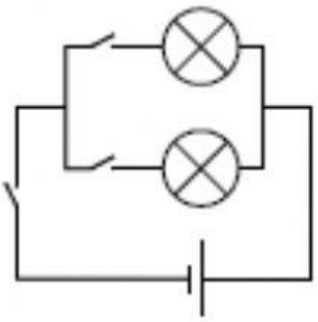
Activity 12

Interactive

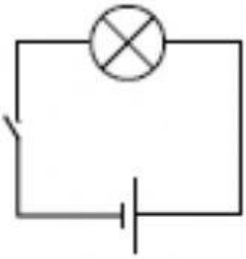

Ahmed and Mariam are enjoying learning about **circuits**.

Help Ahmed to complete the activity that Mariam has created for him. ✓

Circuit Image	Series circuit	Parallel circuit
		
		
		
		

LIVEWORKSHEETS