

Name: _____ Date: _____

Electricity Assessment


1 Look at the set-ups.

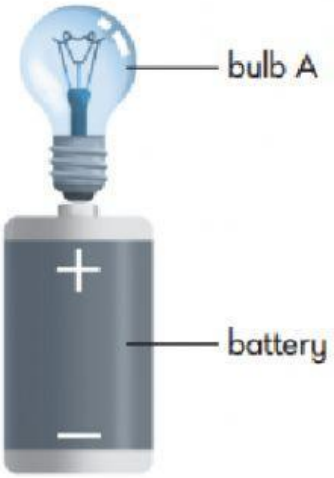

Set-up A

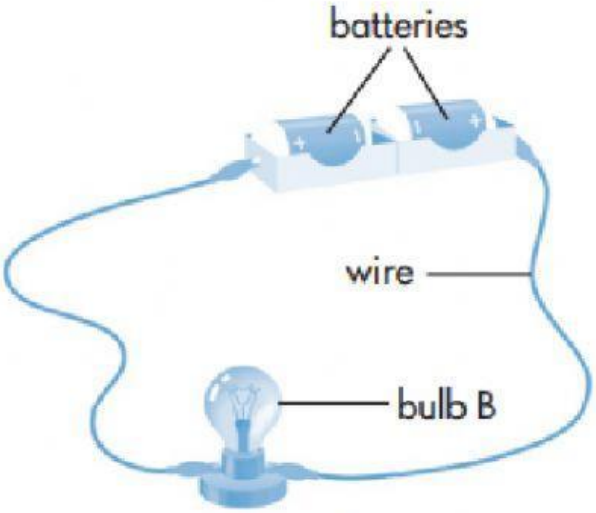

Set-up B

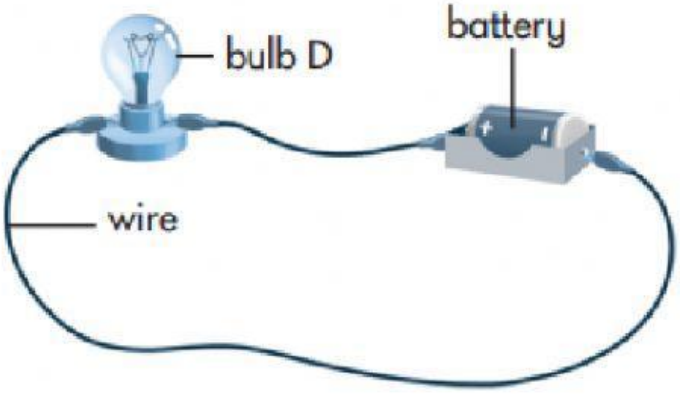

Set-up C

In which set up the bulb will light up? _____

Why? _____

LIVEWORKSHEETS

2 Match the things into what they do in a circuit.



Battery



Wire



Bulb



Buzzer




Battery holder

- Holds the battery
- Uses electricity to make sounds
- Pushes electricity around a circuit
- Connects the parts of a circuit
- Uses electricity to give off light

LIVEWORKSHEETS

3 Look at this circuit.

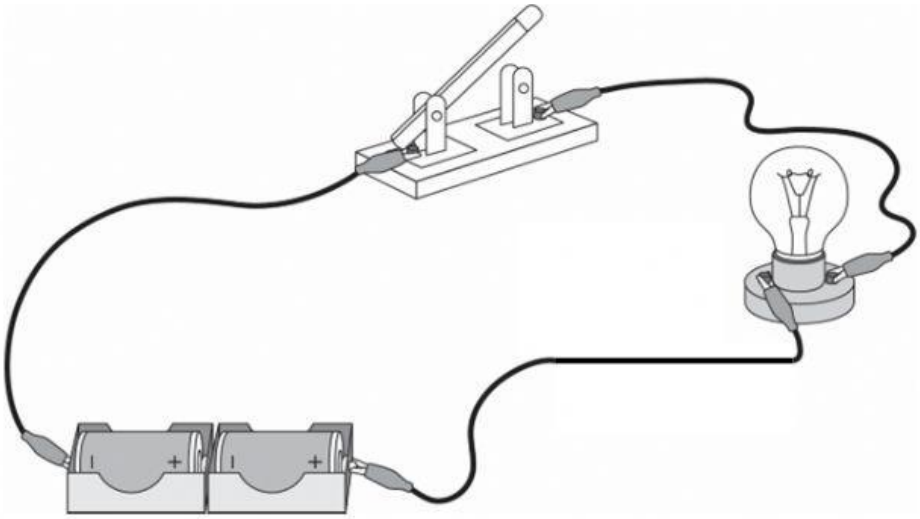

When the switch is open, the bulb will not light up, because _____

The bulb is replaced with a buzzer, what will happen when the switch is closed?

_____

What is the switch used for?

_____

A. I can do the worksheet by myself

B. I need a little help

C. I need a lot of help

LIVEWORKSHEETS