Write your name and your grade _____

Select the name of the following components

Lamp

Cable

Battery

resistor

Lamp

Cable

Switch

resistor

Lamp

Short circuit

Battery

cable

energy

bumb

Battery

cable

Lamp

Short circuit

light

cable

line

cable

switch

circuit

LIVEWORKSHEETS

Select if the circuit are series circuit or parallel circuit

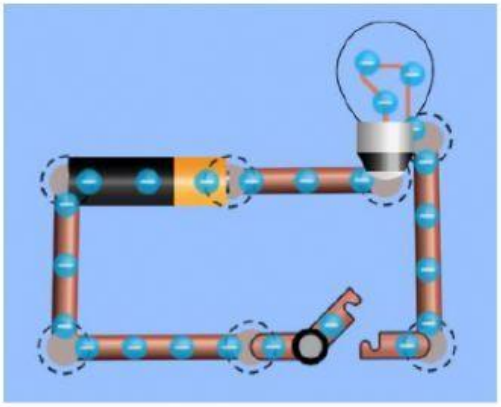

Series

parallel

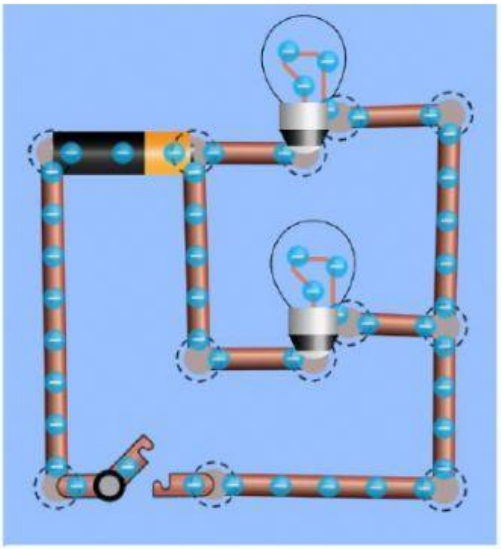

Series

parallel

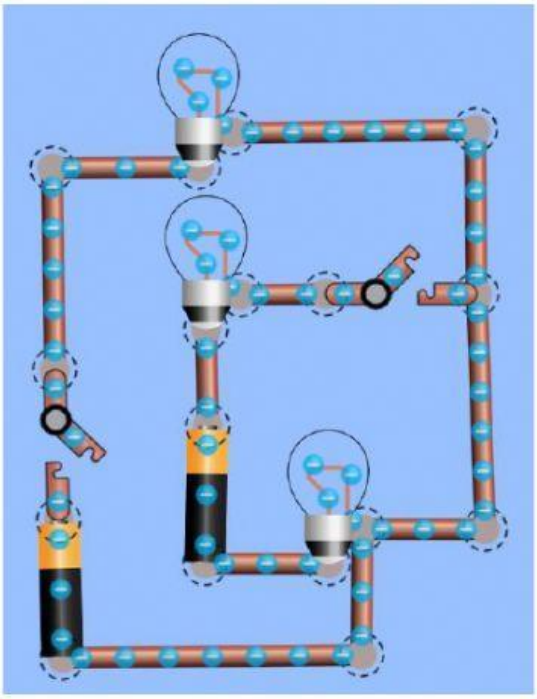

Series

parallel

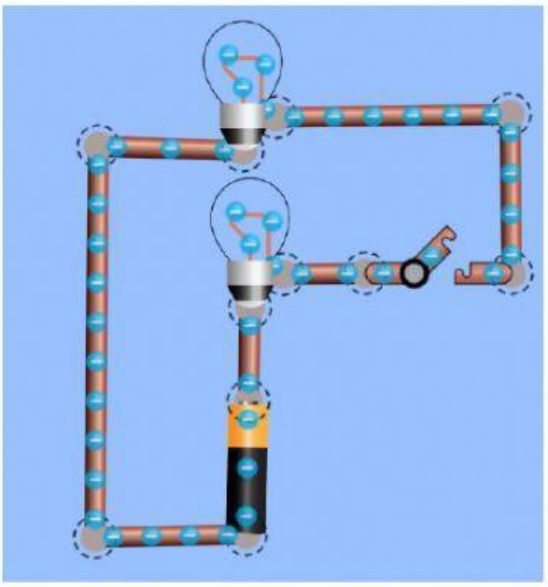

Series

parallel

LIVEWORKSHEETS