Parts of an electrical circuit

What part? Battery , bulb , wire , switch

	Which part?
	
	
	
	

LIVEWORKSHEETS