
Put in order the steps of the experiment of the electrical circuit.

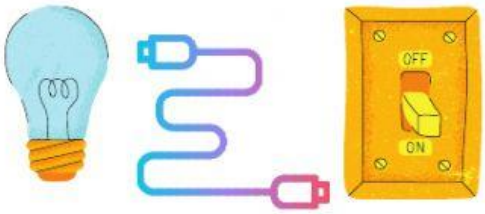Connect a cable to the bottom of the light bulb and connect it to the switch.



EXPERIMENT

Connect one cable to the battery.



QUESTIONS

- **How can you connect all the parts?**
- **How can you turn the light bulb on?**




Screw the light bulb in the bulb holder.



LIVEWORKSHEETS


Connect a cable to the bulb holder.

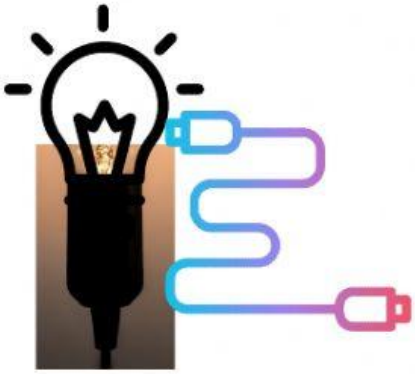

OBSERVATIONS

We have many materials:

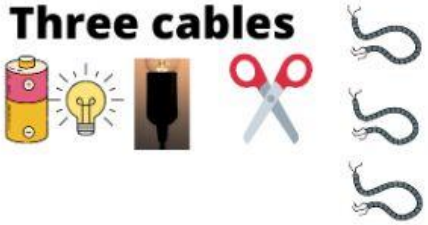
- **A battery**
- **A light bulb**
- **A holder**
- **Scissors**
- **Three cables**



Turn the light bulb on and off.



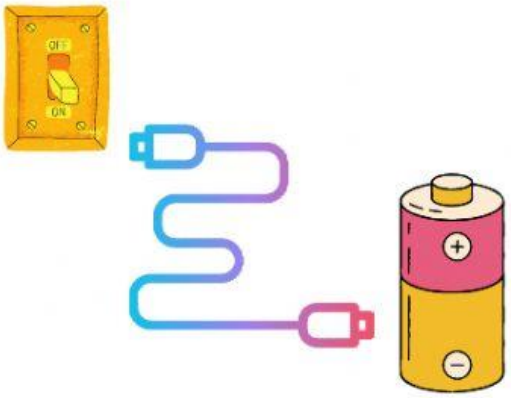Use a cable to connect the switch to the battery.



LIVEWORKSHEETS