
Image below shows part of an electronic circuit. Calculate the value of the current flow if the voltage is 9V and the resistor has a value of 330 ohms. Use the space below to show your working.

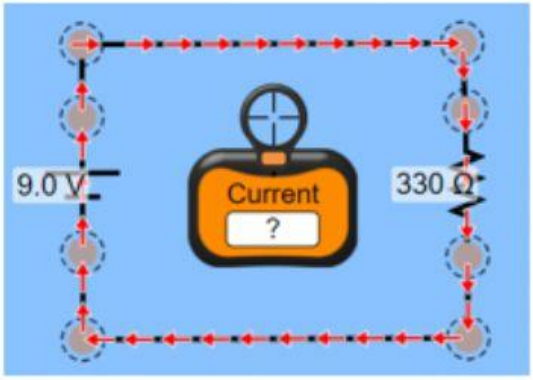Hint: Use V = I x R to find the value of the current flow.



V = I × R
I = V ÷ R
I = 9 ÷ 330
I = 0.027 A

LIVEWORKSHEETS