
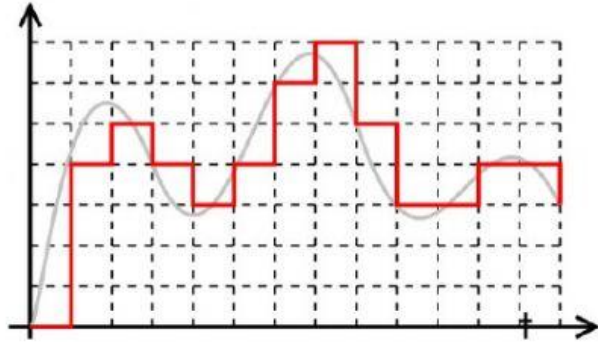


Electrónica digital

1-Di qué tipo de señal es:

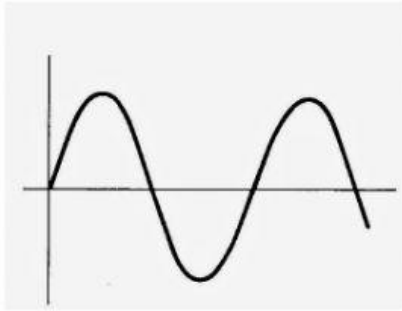

--	--

2-Relaciona con flechas:

10000100

132

111001

4

1001110

21




100

57

10101

78

3-Di qué tipo de puertas son:

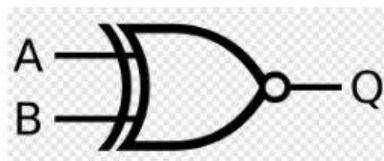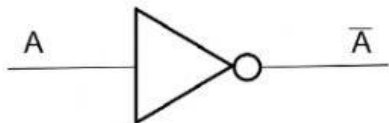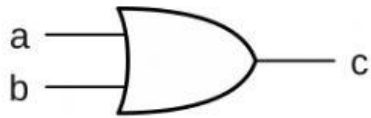

5-Completa la tabla de verdad si se enciende cuando B=0 y C=1

N:	A	B	C	D	S
0	0				
1	0		0	1	
2	0	0	1		
3	0				
4	0			0	
5	0		0		
6	0	1			
7	0		1	1	
8	1		0		
9	1	0			
10	1		1	0	
11	1	0		1	
12	1		0		
13	1				
14	1		1		
15	1	1		1	