Activity 6

Interactive

Label the parts of the **electric circuit** below.
Drag and drop the words provided.

Power source | **Electronic parts** | **Electrical wires**

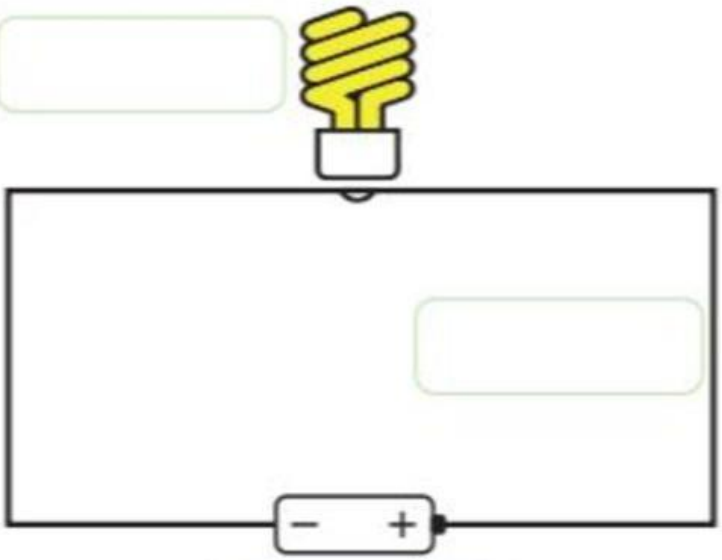

Student Feedback

LIVEWORKSHEETS